



SOUTHEAST UNIVERSITY

Assignment on : BJT Circuit Design

Course Title : Electrical Circuit Design 1

Course Code : EEE241.7

Submitted by

Md.Mahmodul Islam
Dept. of CSE
Batch - 65
ID : 2023200000006


Submitted to

Sajib Biswas Shuvo

Date of Submission
15-01-2025

Problem - 1

ID - 006

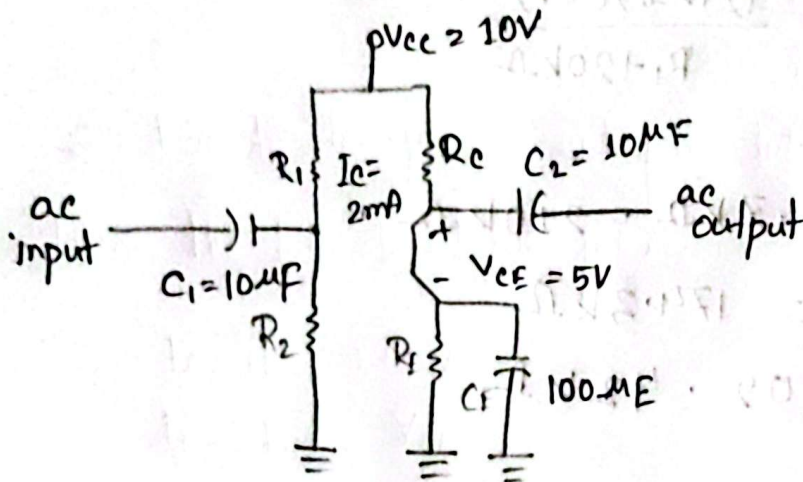

The last 3 digits of my student ~~account~~ ID: 006.

So, sum is = 0 + 0 + 6 = 6

The number is even and I need to solve BC547C.

From google $I_C = 2\text{mA}$, $V_{CE} = 5\text{V}$, $V_{CC} = 10\text{V}$, $\beta = 420(\text{min})$

$$\therefore V_E = \frac{I}{10} V_{CC} = \frac{1}{10} (10\text{V}) = 1\text{V}$$

$$R_E = \frac{V_E}{I_E} \approx \frac{1\text{V}}{2\text{mA}} = 50\Omega$$

$$R_C = \frac{V_{RC}}{I_C} = \frac{V_{CC} - V_{CE} - V_E}{I_C} = \frac{10 - 5 - 1}{2\text{mA}}$$

$$V_B = V_{BE} + V_E = 0.7\text{V} + 1\text{V} = 1.7\text{V}$$

$$R_2 \leq \frac{1}{10} \beta R_E$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

Sub:

Sat ☐ Sun ☐ Mon ☐ Tue ☐ Wed ☐ Thu ☐ Fri ☐

Time: Date: / /

$$R_2 \leq \frac{1}{10} (420) \times (0.5 \text{ k}\Omega) = 20 \text{ k}\Omega$$

$$V_B = 1.7 \text{ V} = \frac{(21 \text{ k}\Omega)(10 \text{ V})}{R_1 + 20 \text{ k}\Omega}$$

On,

$$1.7 R + 35.7 \text{ k}\Omega = 210 \text{ k}\Omega$$

$$1.7 R_1 = 174.3 \text{ k}\Omega$$

$$R_1 = 102.42 \text{ k}\Omega$$

$$\therefore R_E = 500 \text{ k}\Omega$$

$$R_C = 2 \text{ k}\Omega$$

$$R_1 = 102 \text{ k}\Omega$$

$$R_2 = 20 \text{ k}\Omega$$

$$V_1 (\text{VOLT}) = \dots$$

$$\dots = \frac{V_1}{V_2}$$

$$V_1 + V_2 = \dots$$

$$V_1 + V_2 + V_3 + V_4 + V_5 = \dots$$

Problem-2 ID-006

Sum of the last 3 digits = $0+0+6$
 $= 6$; it's even

So, I've to design 9V relay module,
 from the data sheet we get,

$$I_{c sat} = 50mA$$

$$I_{c sat} = \frac{V_{cc}}{R_c}$$

$$\Rightarrow 50 \times 10^{-3} = \frac{5}{R_c}$$

$$\Rightarrow R_c = \frac{5}{50 \times 10^{-3}}$$

$$\therefore R_c = 100\Omega$$

$$I_{c'} = \frac{I_{c sat}}{\beta} = \frac{50 \times 10^{-3}}{135}$$

$$\beta = 135$$

$$= 370.37 \mu A$$

$$I_B > I_{B'}$$

Let,

$$I_B = 740.74 \mu A$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_B}$$


$$\Rightarrow 740.74 \times 10^{-6} = \frac{5 - 0.7}{R_B}$$

$$\therefore R_B = 5805 \Omega$$

Sub :

Sat ☐ Sun ☐ Mon ☐ Tue ☐ Wed ☐ Thu ☐ Fri ☐

Time : Date : / /

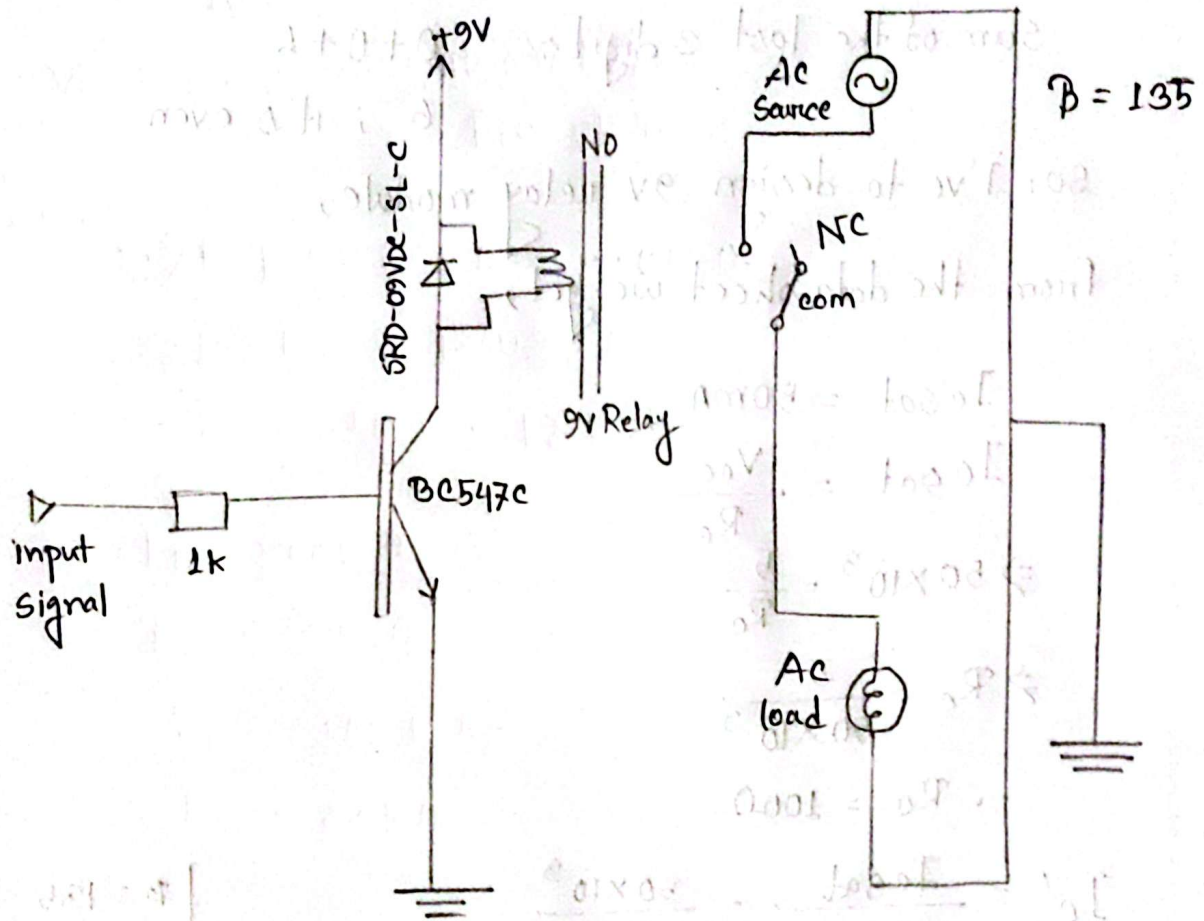

NOTE: Relay model number = SRD-09VDC-SL-C

Resistor values: $R_B = 5805\Omega$, $R_C = 100\Omega$

$V_{CC} = 5V$

P/N names :
(i) Signal
(ii) Ground
(iii) V_{CC}

JPS